


Basics of Engineering

PN junction Diode VI characteristics


SPARKSACADEMY

Types of materials

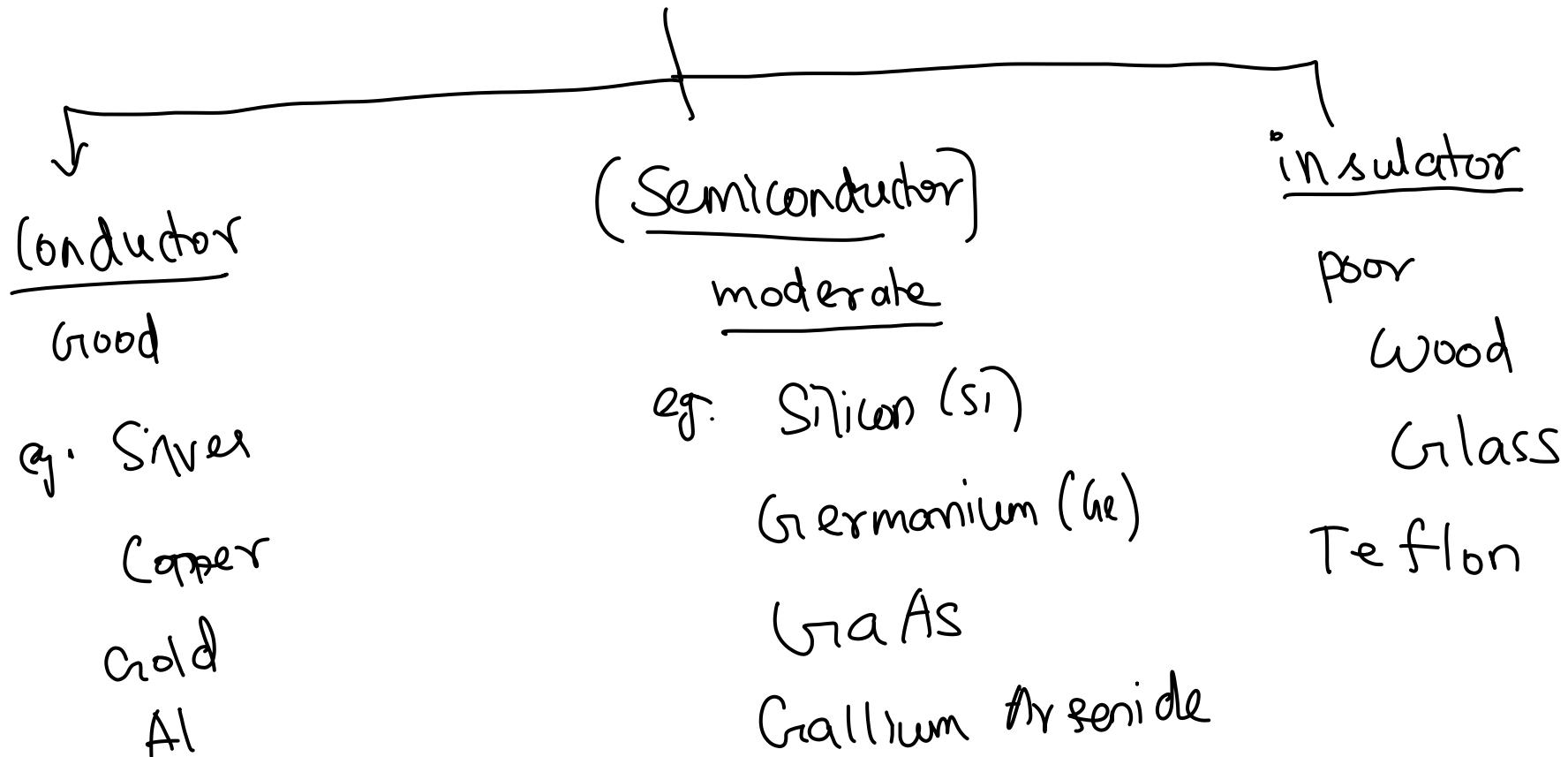Conductivity $\rightarrow$ flow of charges Unit of conductivity $\Rightarrow$ Siemens/meter (S/m)



SC

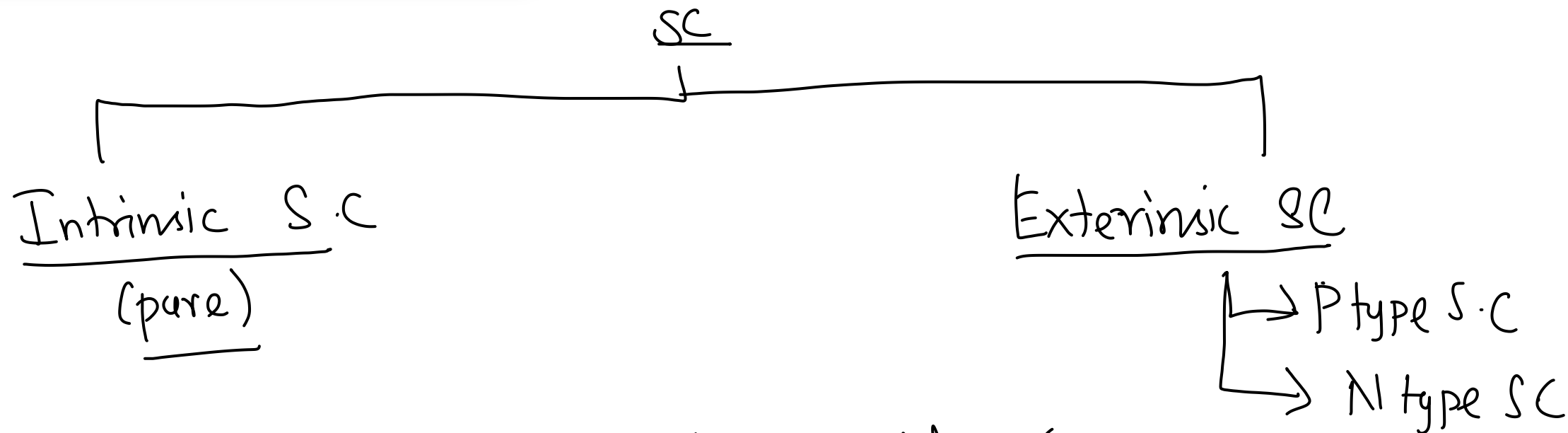

Doping :- The process of adding (impurities) to change conductivity.

Dopend :-

- / P type
- / n type




P type Semiconductor

Trivalent Atoms



o + → holes
- → electron


Al
Boron
Gallium

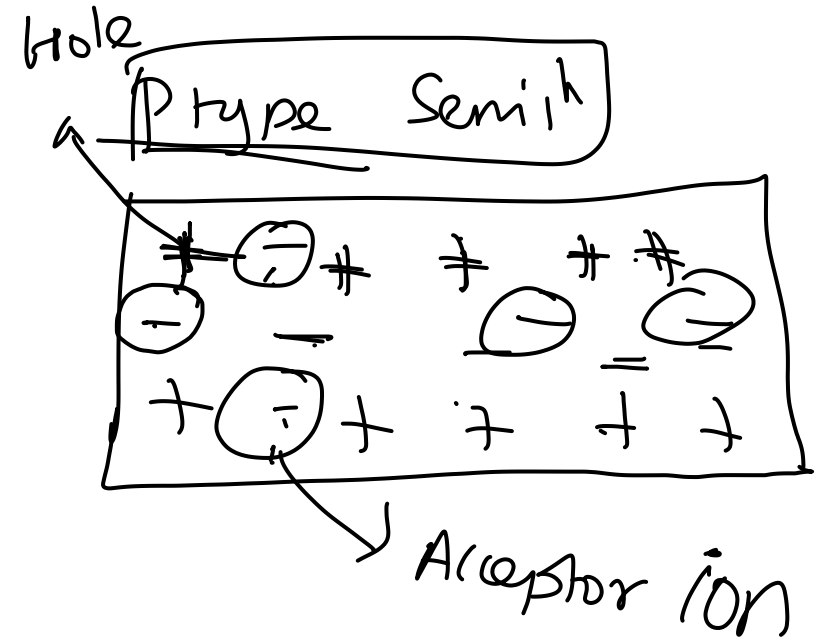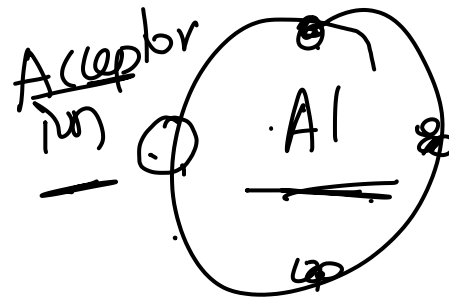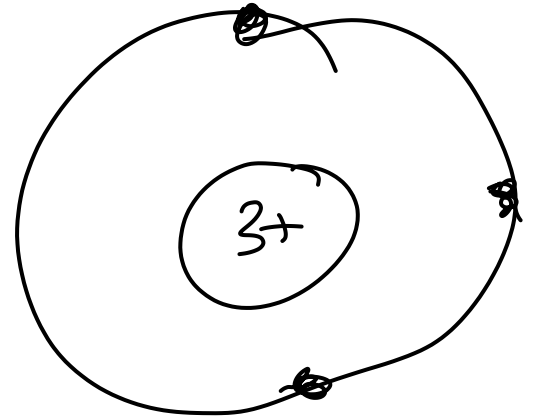




n type Semiconductor.

Pentavalent

Atom

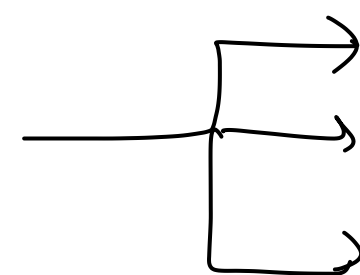

Arsenic
Antimony
phosphorus.

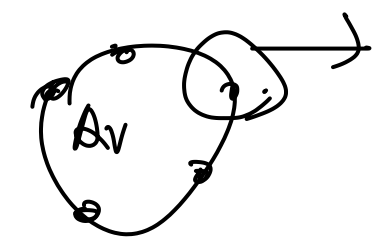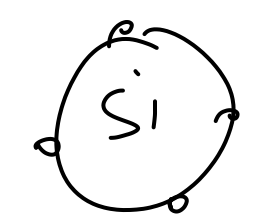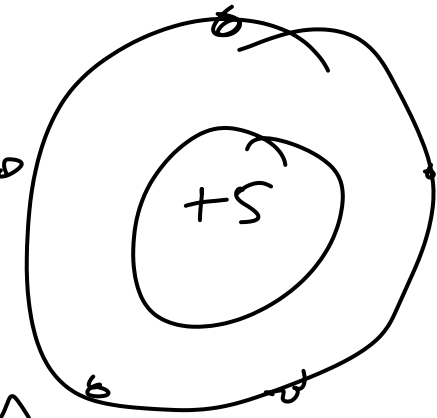


Donor ion

n type

Minority carrier
(holes)

Donor ion

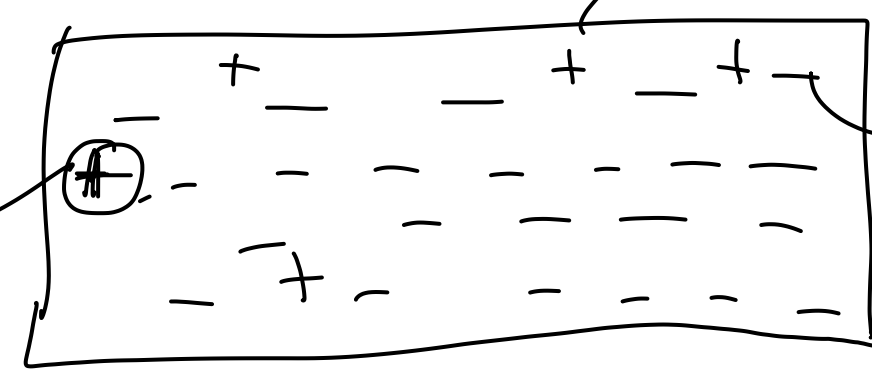


Majority
carrier


PN Junction Diode

I_{ideal}

VI characteristics:- Forward Bias

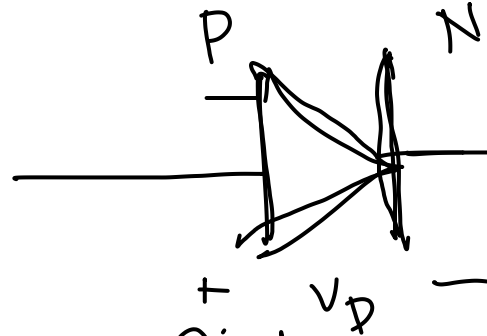




Current = 0

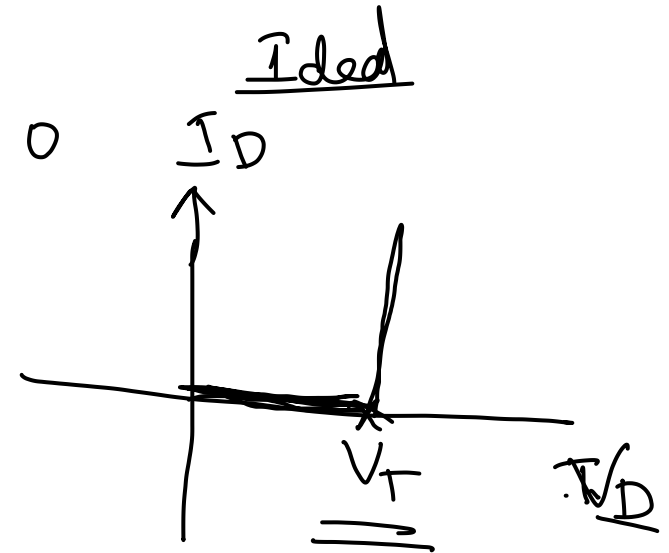


$V_T \rightarrow$ Threshold
 $V_T \approx 0.7\text{V}$

Cut in V_T

Reverse Bias:

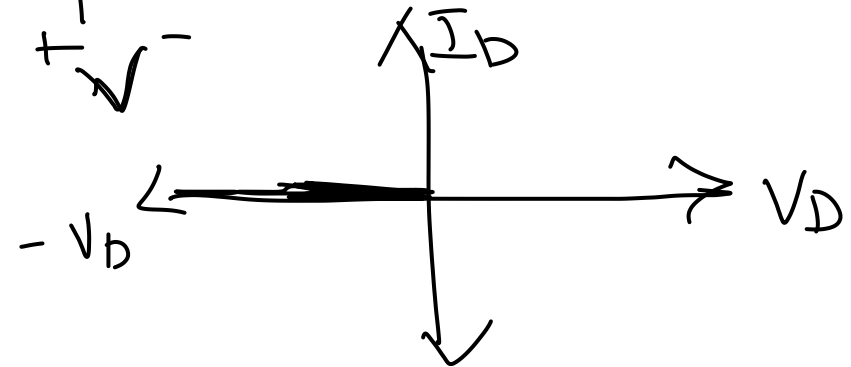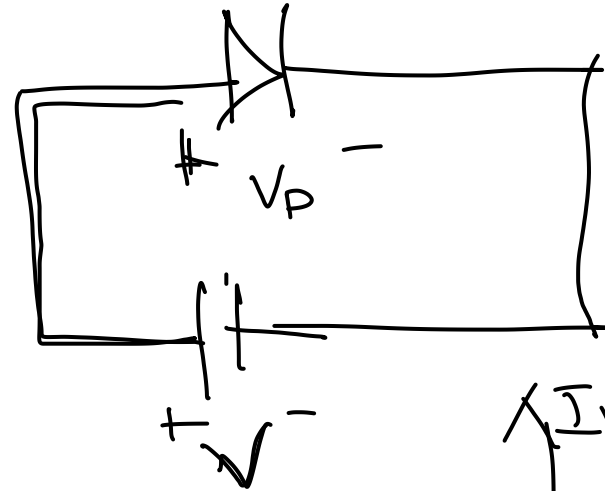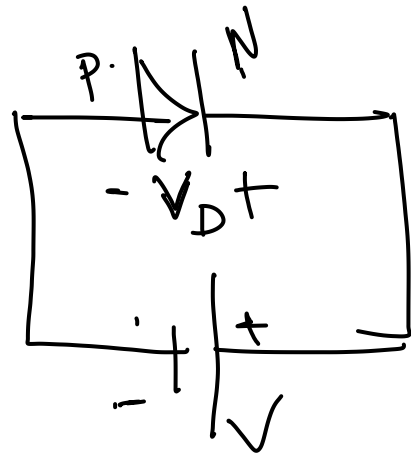

p-type $\lesssim$ n-type

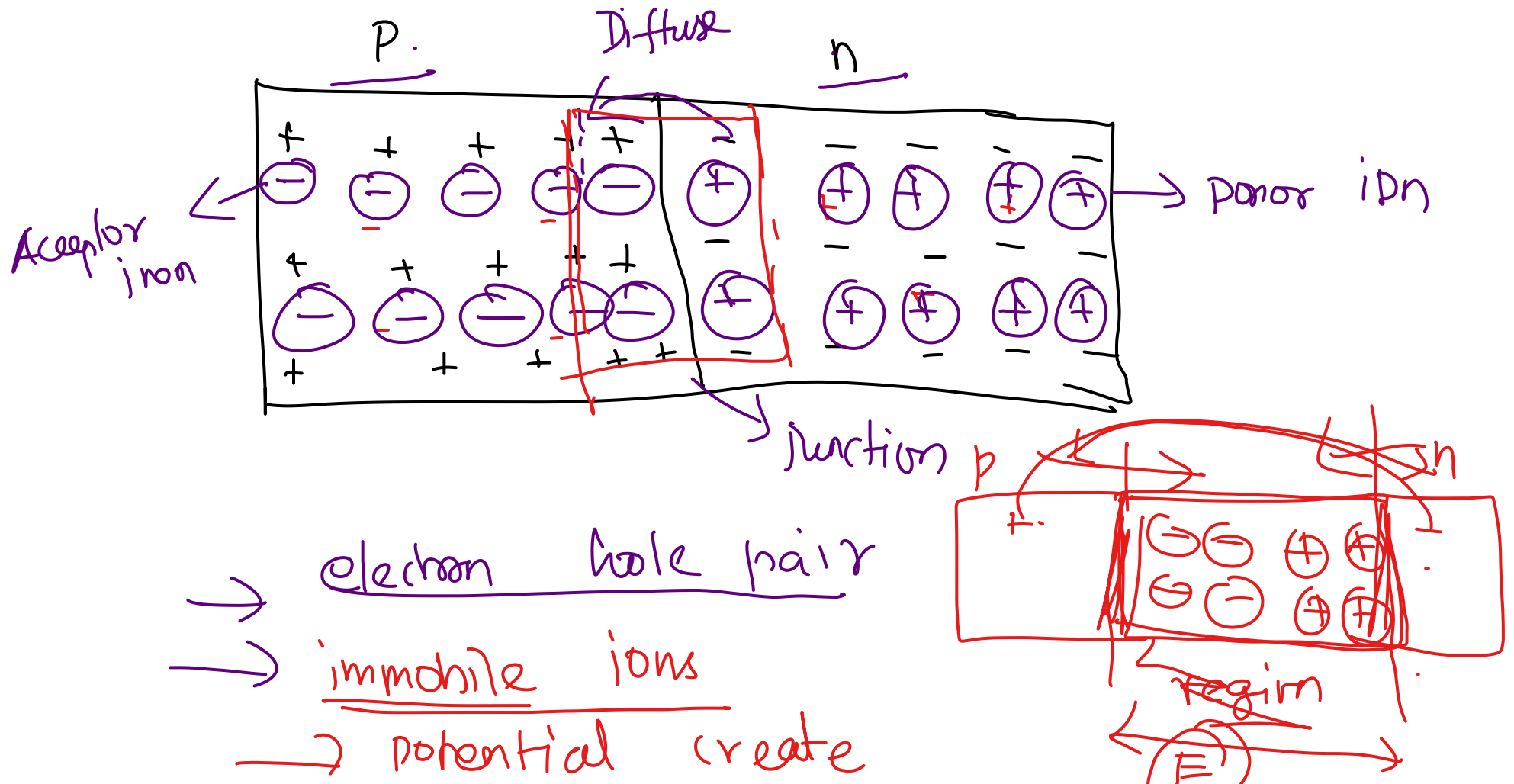


Depletion Region

→ Depletion region

→ Built in V_{tg} / Built in potential.

→ cut off V_{tg}

→ Barrier

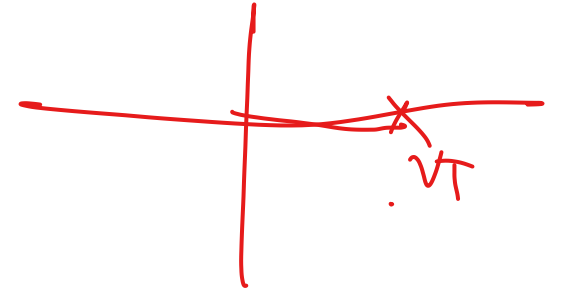

Barrier potential



→ over all current = 0

no external Bias



$$\begin{aligned} G_i &= 0.7 \text{ V} \\ G_R &= 0.3 \text{ V} \end{aligned}$$


Biasing

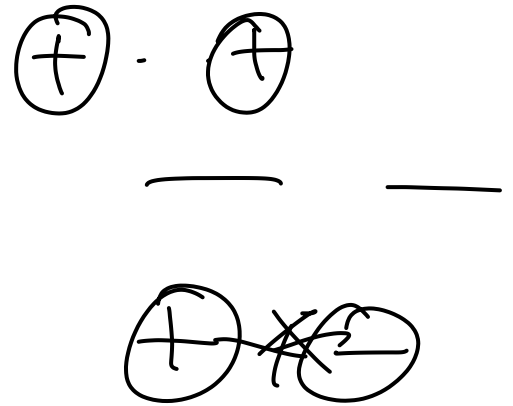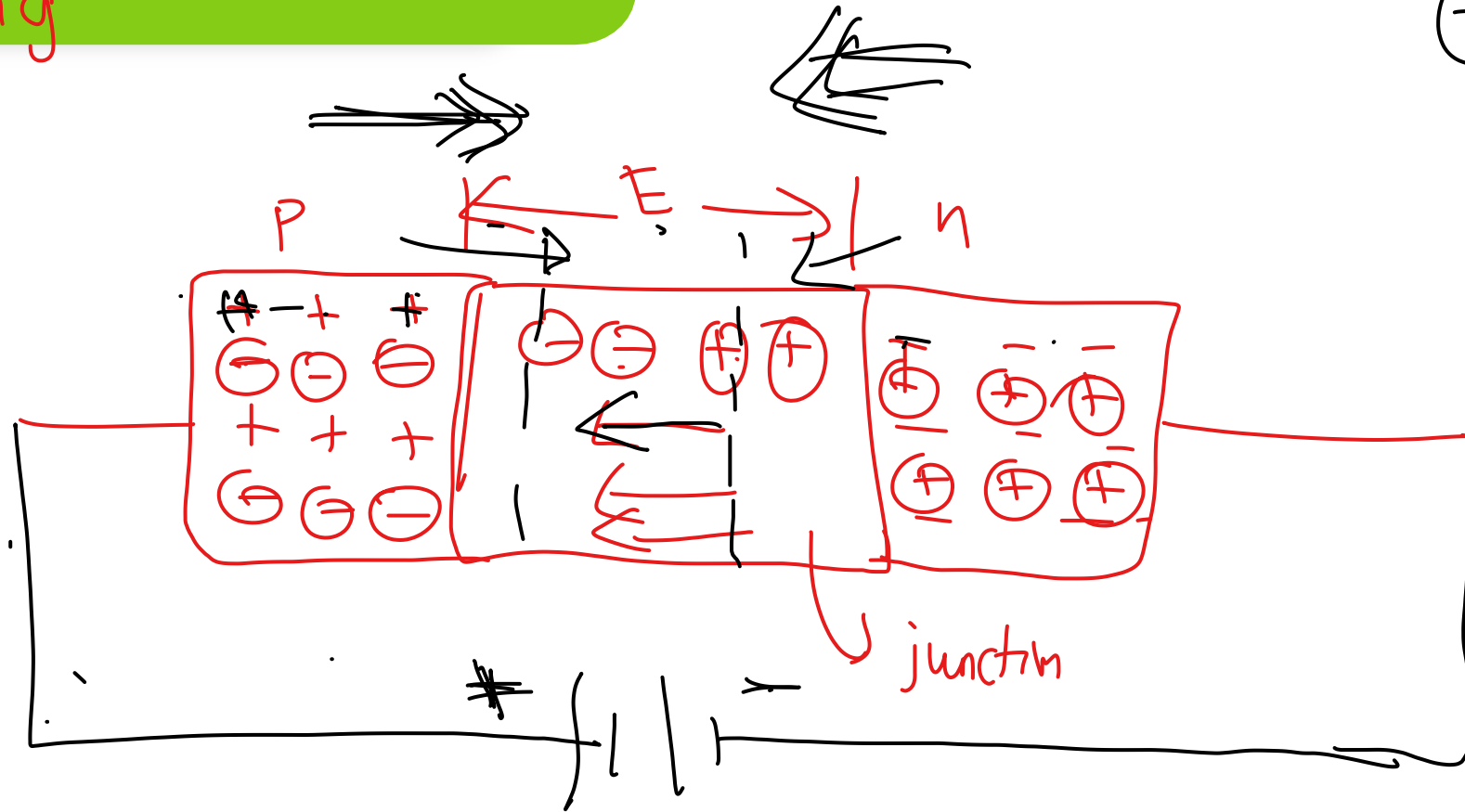


0.7V

forward Majority carrier

V_I

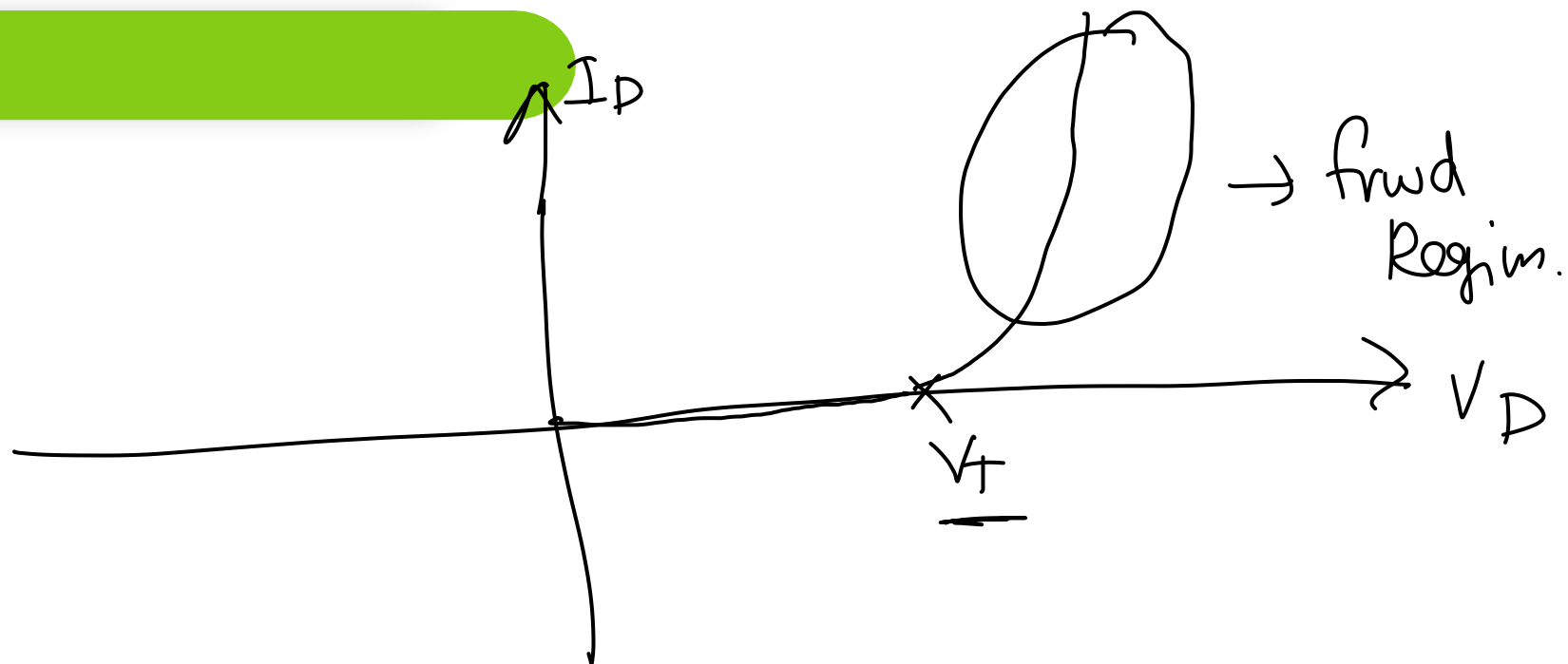


Reverse Bias.

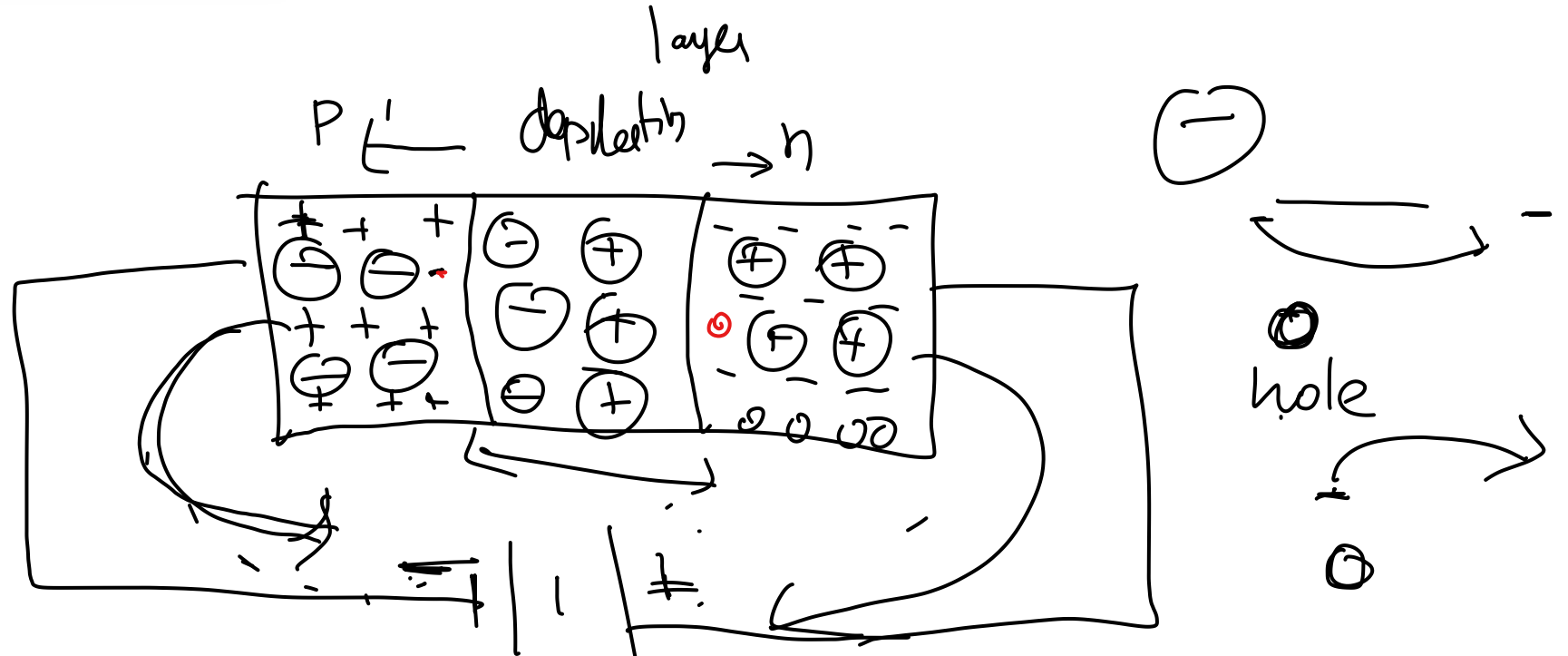


Reverse

Saturation
(current) I_s

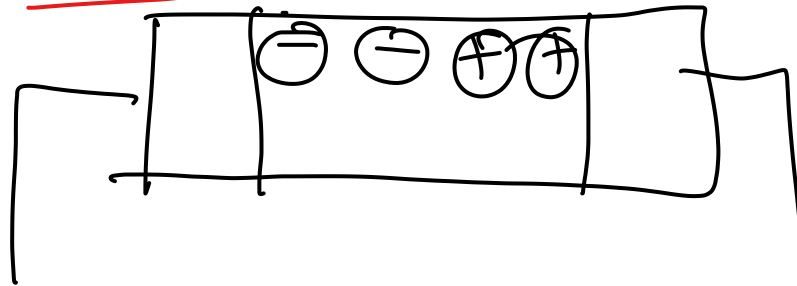

V_B

VI

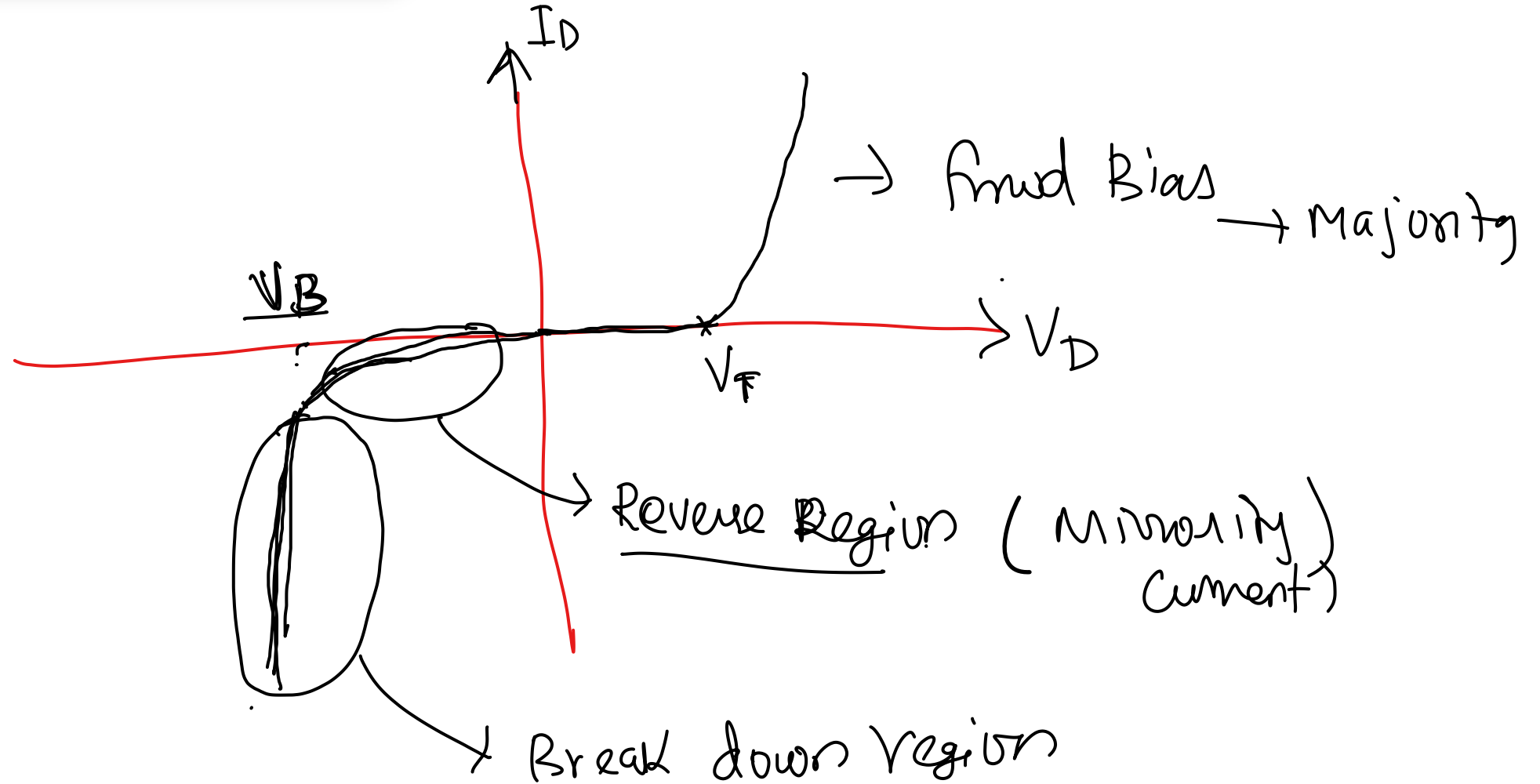


Basics of Engineering

Zener Diode

SPARKS ACADEMY

VI
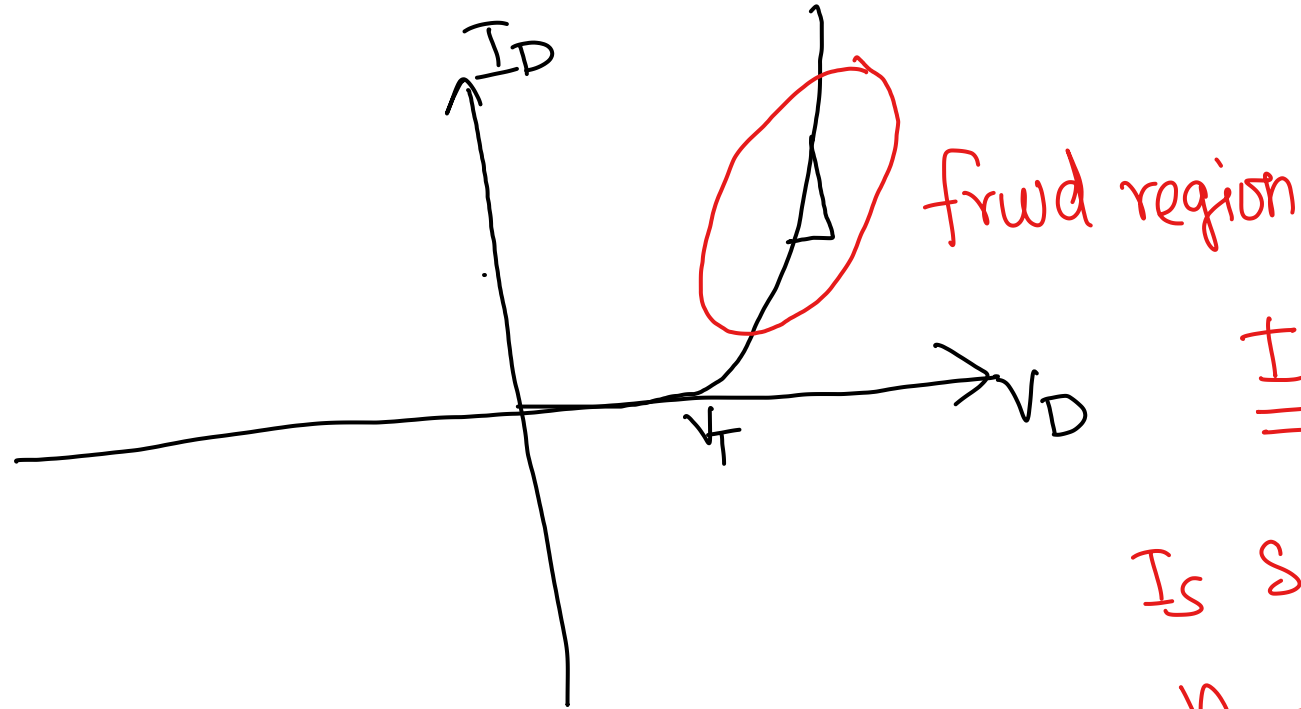
$$\underline{\underline{R_D}} = \frac{V_D}{I_D}$$



$$\underline{\underline{I_D}} = \underline{\underline{I_S}} \left[e^{\frac{V_D}{\eta V_T}} - 1 \right]$$

I_S Saturation current
 η - ideality factor
 $V_D - V_T$ diode

$V_T \rightarrow$ Thermal Voltage
 $V_T \propto T$



.


$$\underline{V_T} = \frac{kT}{q}$$

k boltzmann's constant $(1.38 \times 10^{-23} \text{ J/K})$

T - Temperature

q - charge of electron $(1.6 \times 10^{-19} \text{ C})$



Reverse Bias

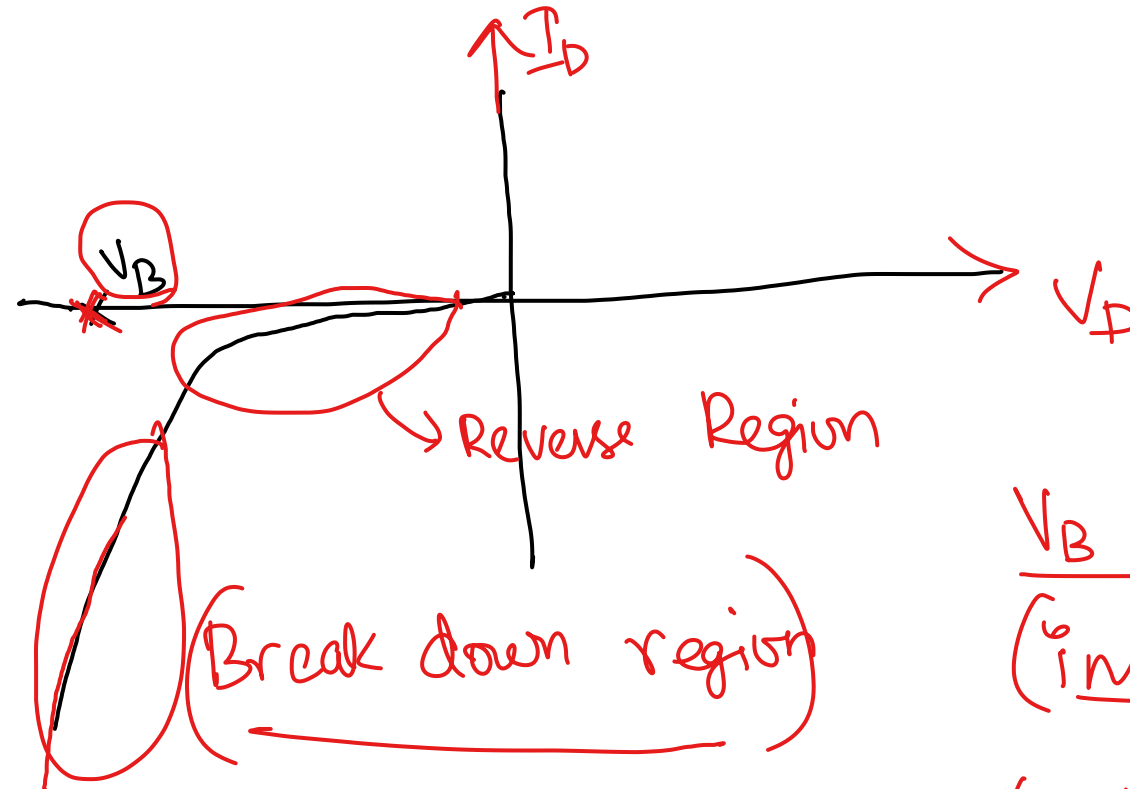

V_B Break down V_{tg}
(impact ionization)

Avalanche effect
Avalanche Break down

Zener diode

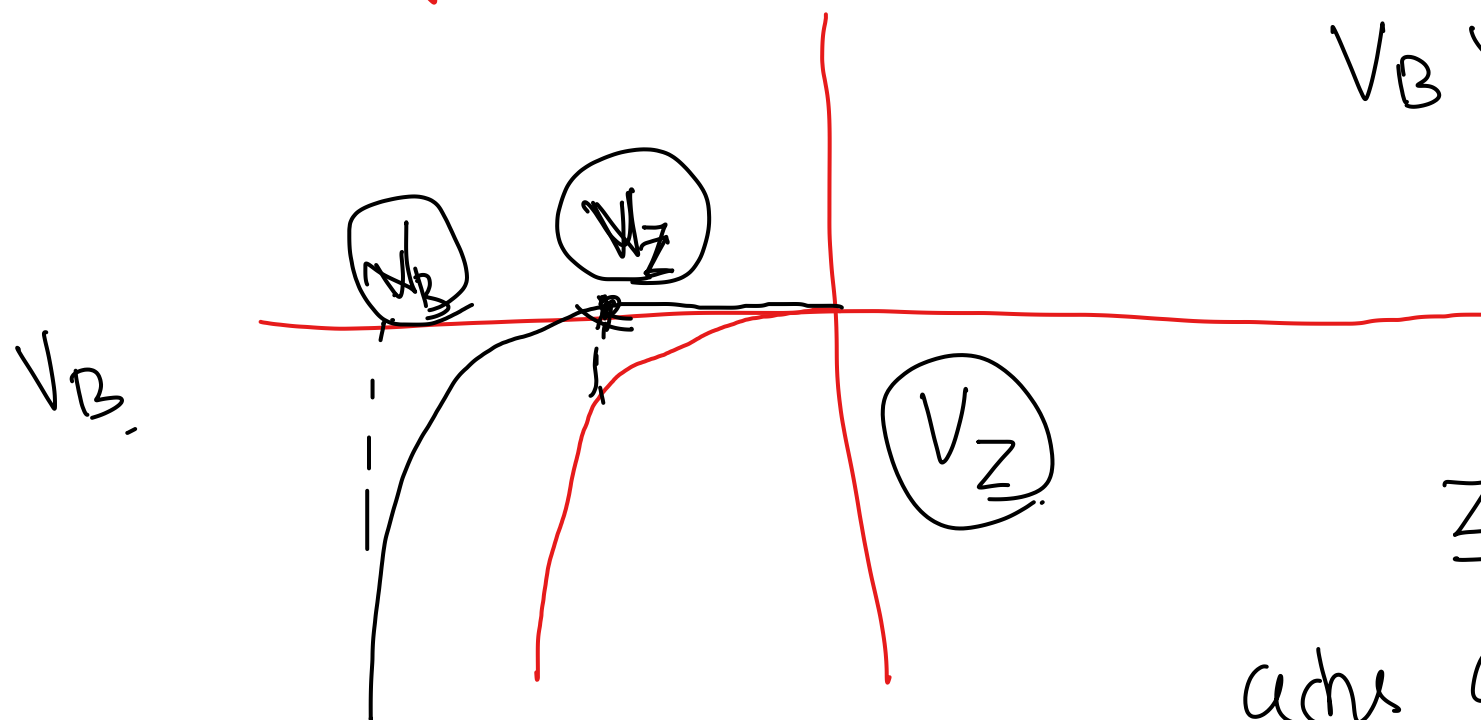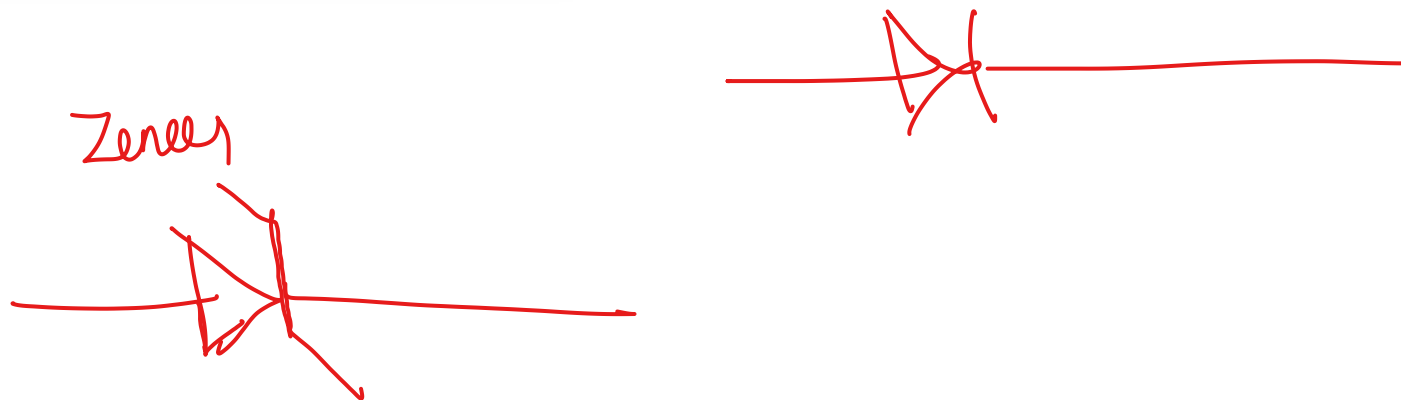

$$V_B > \underline{\underline{V_Z}}$$

$$\underline{\underline{10V}}$$

$$\textcircled{V_Z}$$



$$\textcircled{6V}$$

$$\underline{\underline{V_Z}}$$

Zener diode

acts as a voltage regulator

Pn diode.

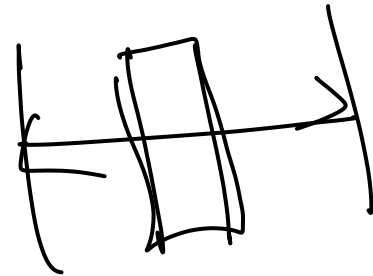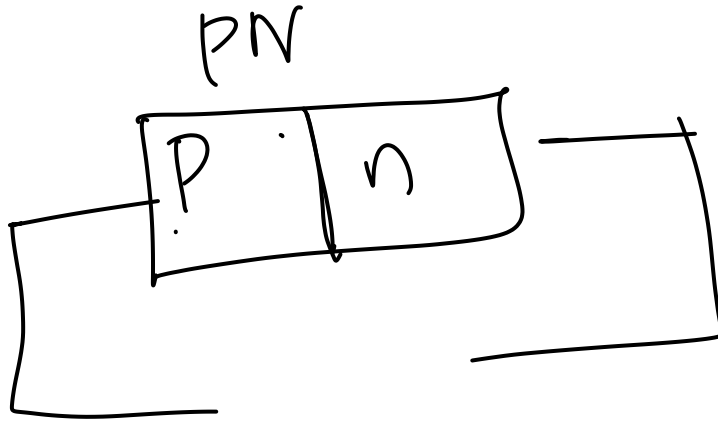

Zener diode



p^+ $\rightarrow$ heavily doped

n^+ $\rightarrow$



Basics of Engineering

Half Wave and Full Wave Rectifier

SPARKS ACADEMY


Diode - VI

ideal

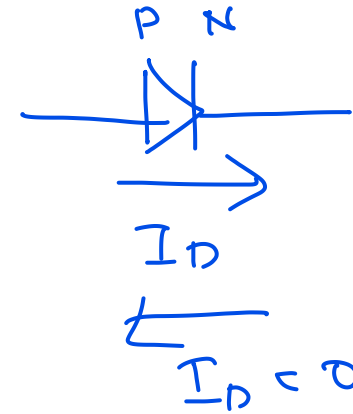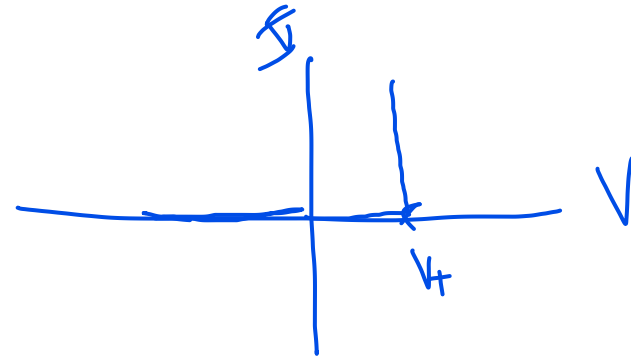


forward Bias

I_D

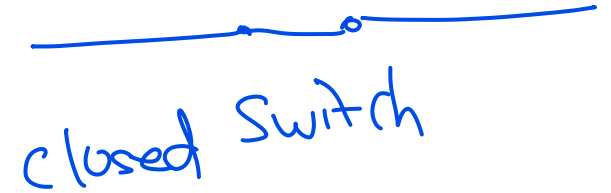

Reverse Bias $I_D = 0$

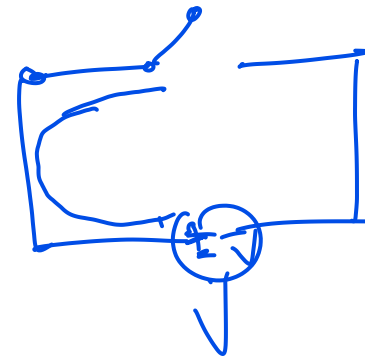

open switch


PN

Rectification:-


Ac signal to DC signal

Rectification $\Rightarrow$

Ac

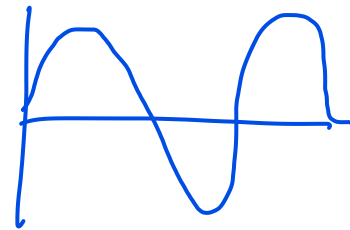


to DC

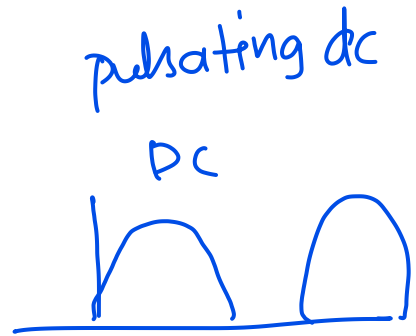


Rectifier:-



Types of Rectifier.

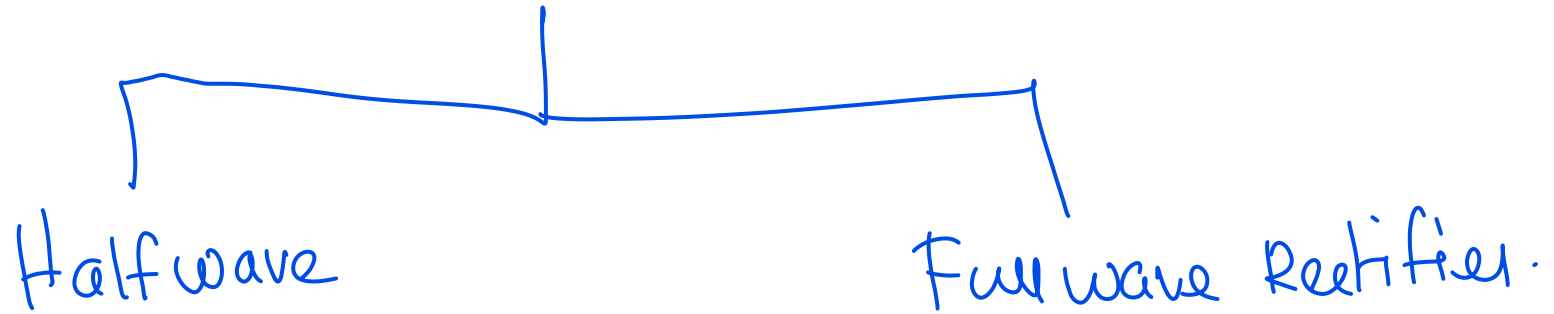


Halfwave Rectifier:-

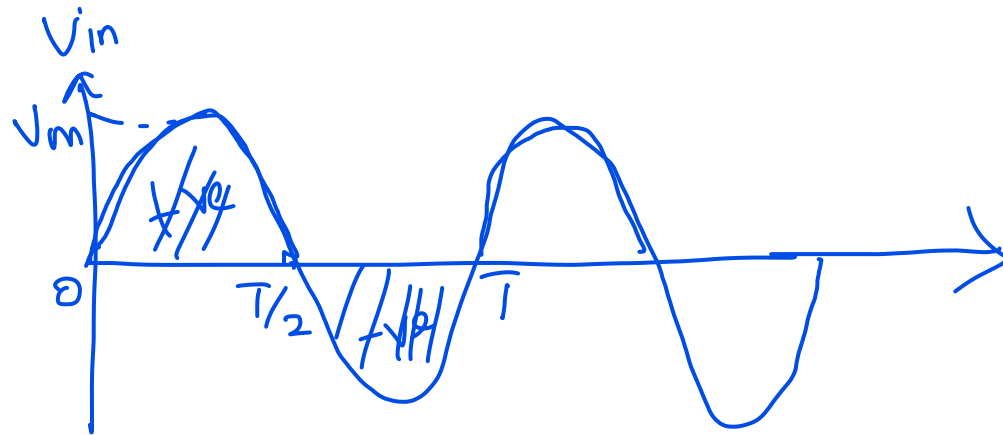


$\Rightarrow$



$\Rightarrow$

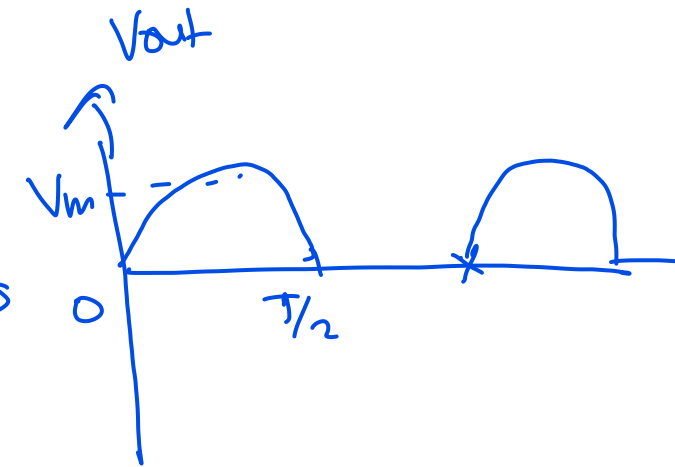


ckt Diagram

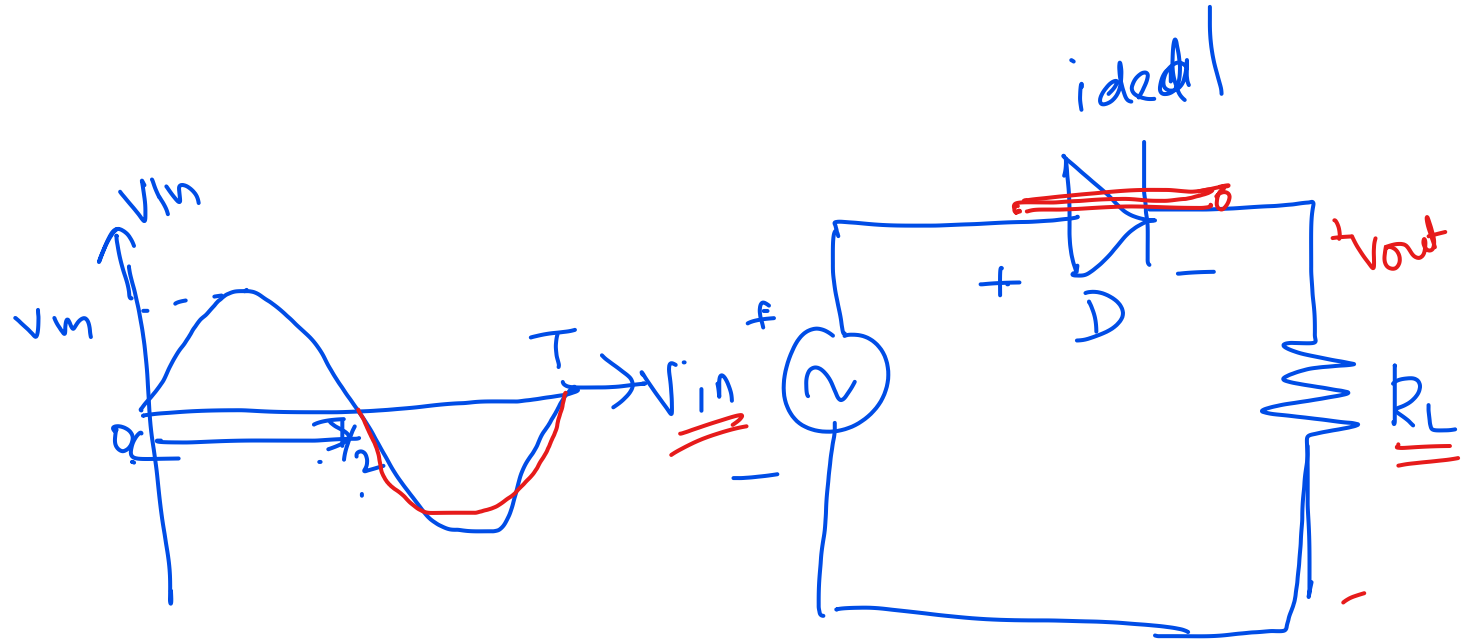



1st half cycle

D is frwd Bias
↳ closed switch

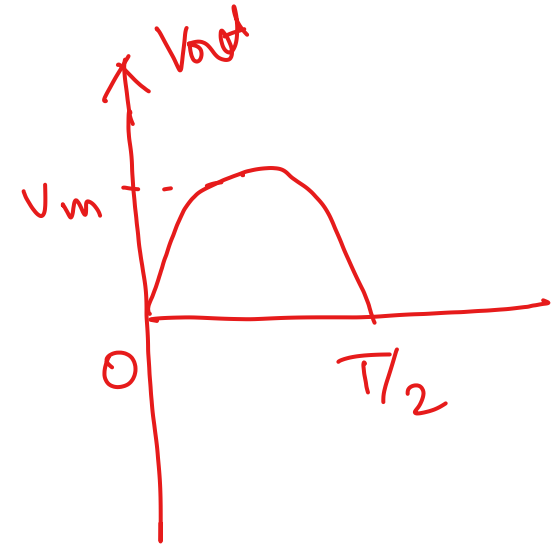


2nd half cycle.

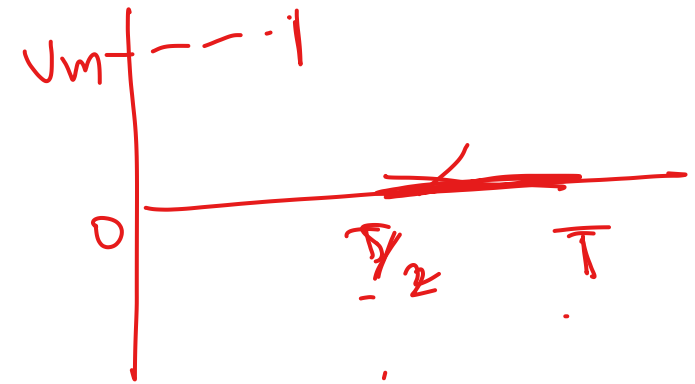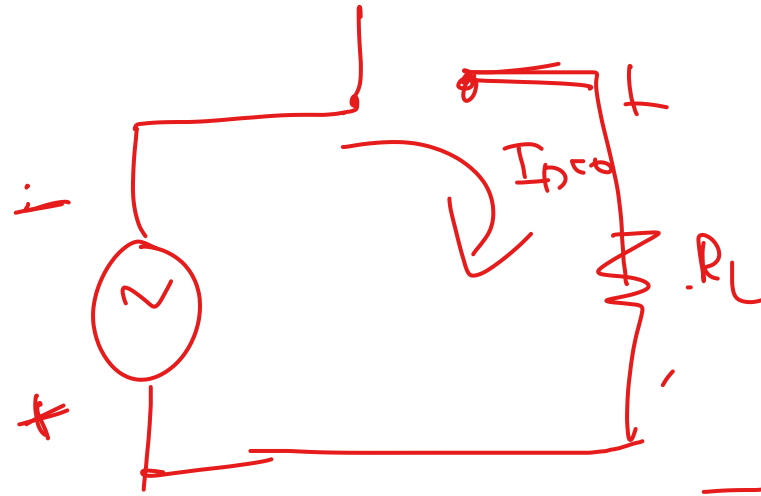Reverse Bias. $\Rightarrow$ Open switch $\rightarrow I_D = 0$



O/p wave form

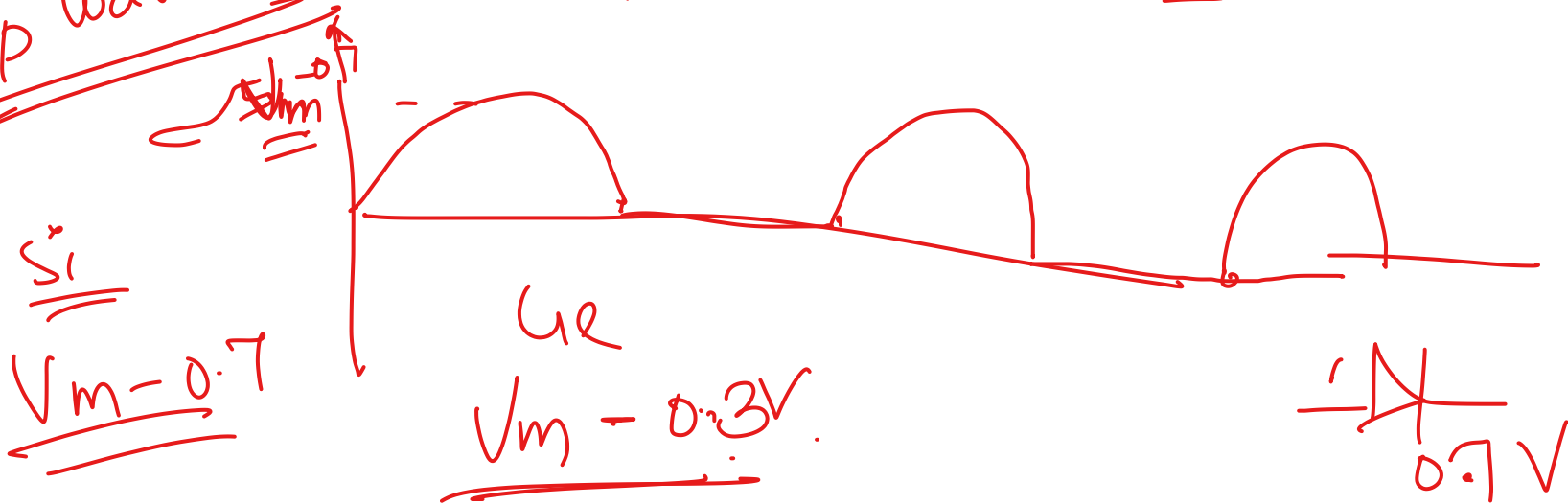

Ideal
Non Ideal
Veg drop



Performance:-

(dc value)


1) Average value:-

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt$$




$$V_{avg} = \frac{V_m}{\pi}$$

$$I_{avg} = \frac{I_m}{\pi}$$

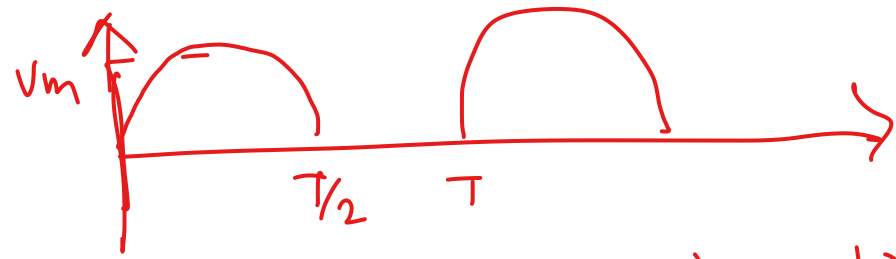
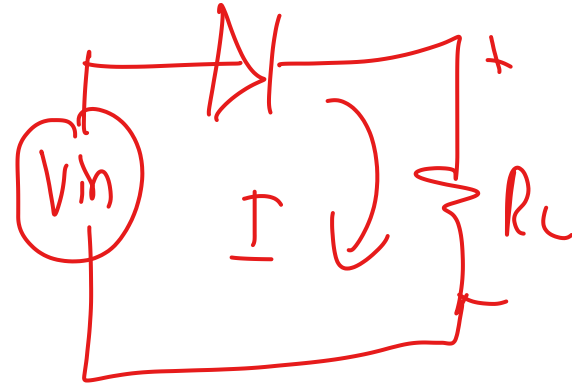
$$v(t) = \begin{cases} V_m \sin(\omega t) & 0 < t < T/2 \\ 0 & T/2 < t < T \end{cases}$$



$$\underline{\underline{i(t)}} = \begin{cases} I_m \sin \omega t & 0 < t < T/2 \\ 0 & T/2 < t < T \end{cases}$$

2)

RMS Value

$$V_{rms} = \frac{1}{T} \left[\int_0^T v^2(t) dt \right]^{1/2}$$

(X)

$$\underline{V_{rms}} = \underline{V_m} / 2$$

$$I_{rms} = I_m / 2$$

$$I_m = \frac{V_m}{R_L}$$




$$I_{avg} = \frac{I_m}{\pi} = \frac{V_m}{\pi R_L}$$

3) Peak Inverse Voltage PIV:-

$\Rightarrow$ RB maximum Vtg $\Rightarrow$ PIV

Half wave


$$PIV = V_m$$

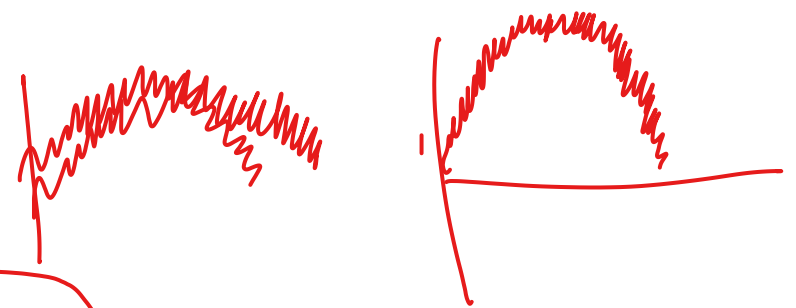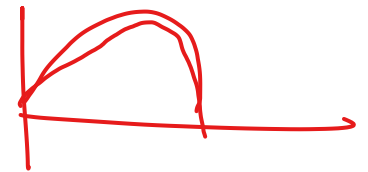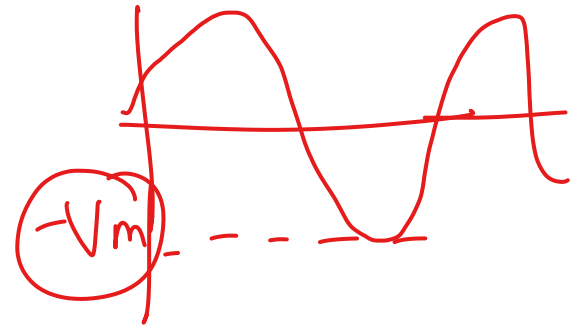

4) Ripple factor:-

$$r = \frac{I_{rmm}}{I_{DC}} = \underline{\underline{1.21}}$$

filter circuit

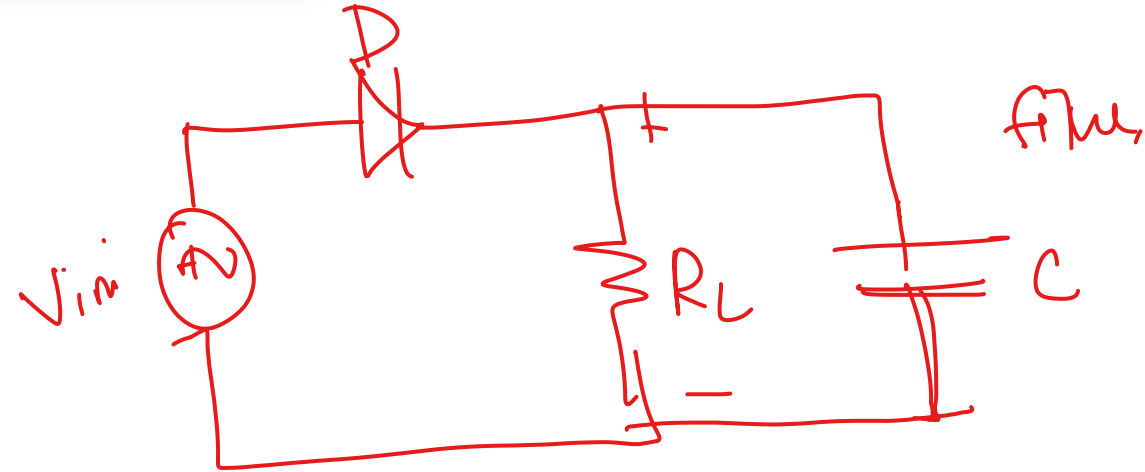

2) efficiency :-

$$\eta = \frac{\text{DC Output power}}{\text{AC Input power}}$$

$$\eta = 40.6 \%$$

Application .

$\Rightarrow$ AC to DC Conversion
 $\Rightarrow$ Demodulation

$$PIV = V_m$$

$$\text{Output frequency} = f$$




$$\text{ripple factor} = 1.21$$

$$\eta = 40.6\%$$

$$RMS = \frac{V_m}{2}$$

$$\text{Average Value (dc value)} = \frac{V_m}{\pi}$$


Full Wave Rectifier:

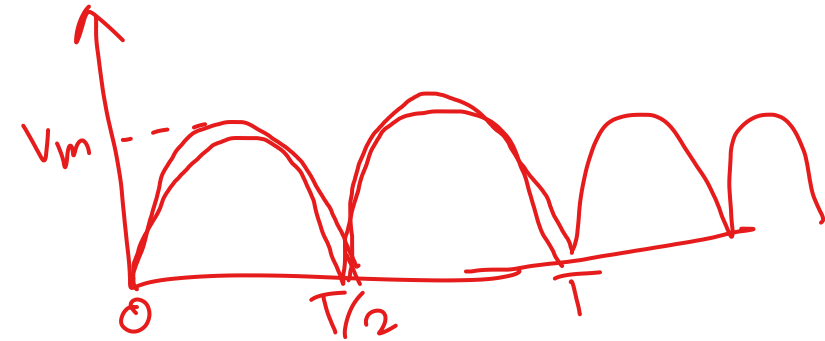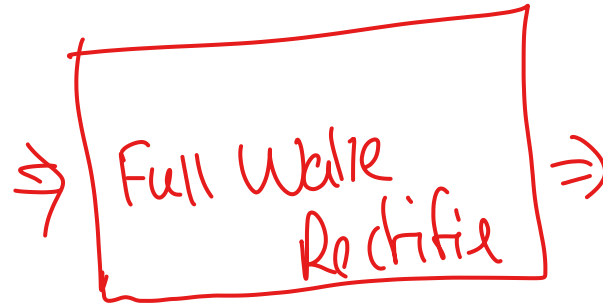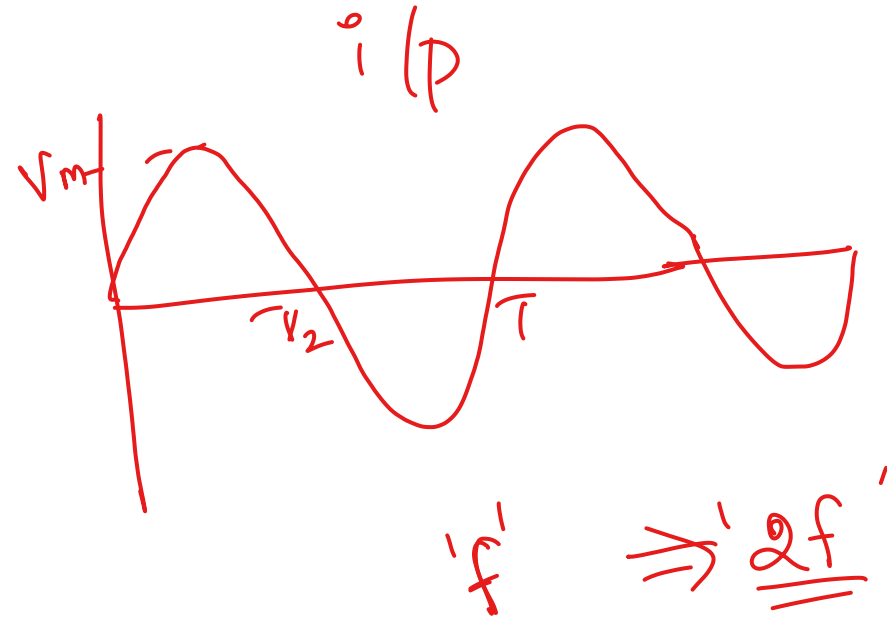

$$T' = T/2$$




$$f' = \underline{\underline{2f}}$$

2 Methods

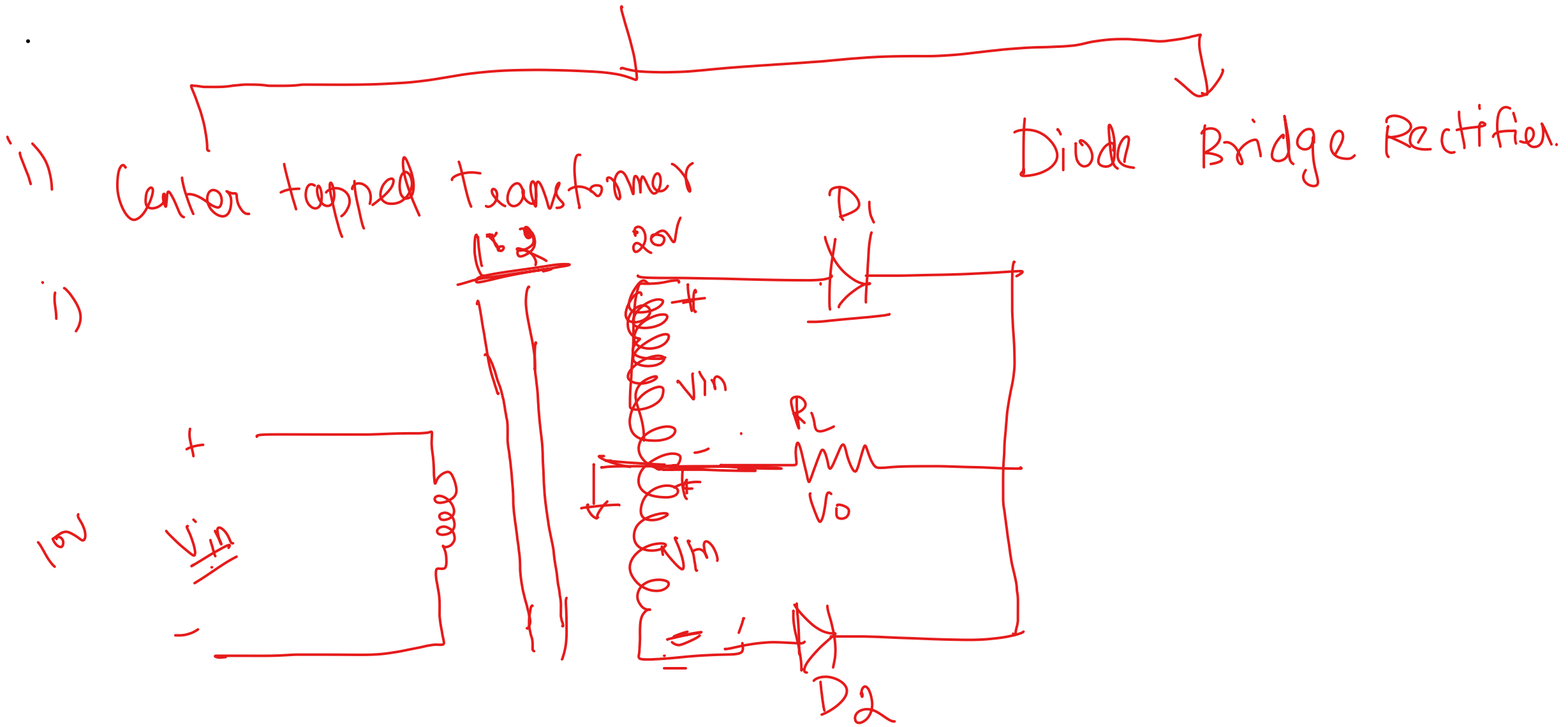

Center tapped Transformer:

ideal

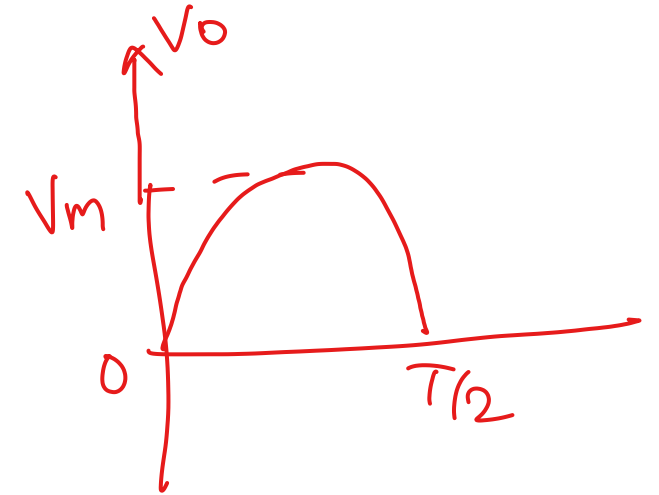
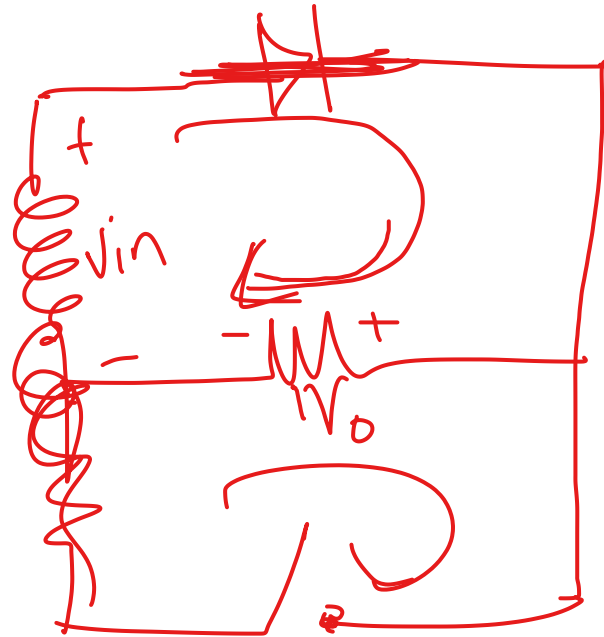
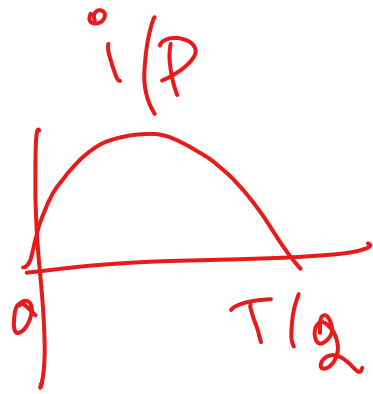


1st half cycle $D_1 - FB \Rightarrow \underline{\text{closed}} \Rightarrow I_n$
 $D_2 \rightarrow RB \rightarrow \underline{\text{open}} \quad \text{--- } X$

2nd half cycle

$\hookrightarrow \underline{D_2 \rightarrow FB} \rightarrow \text{closed}$

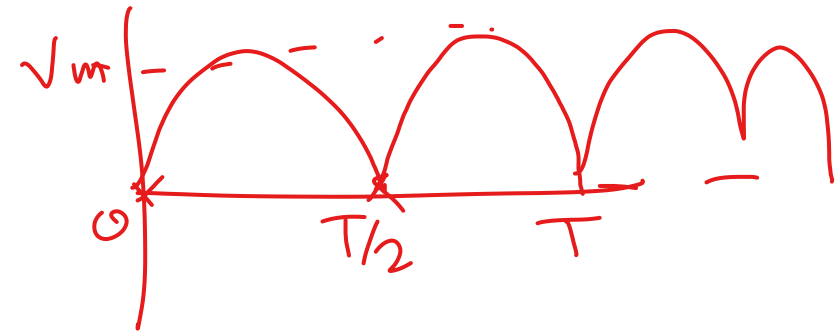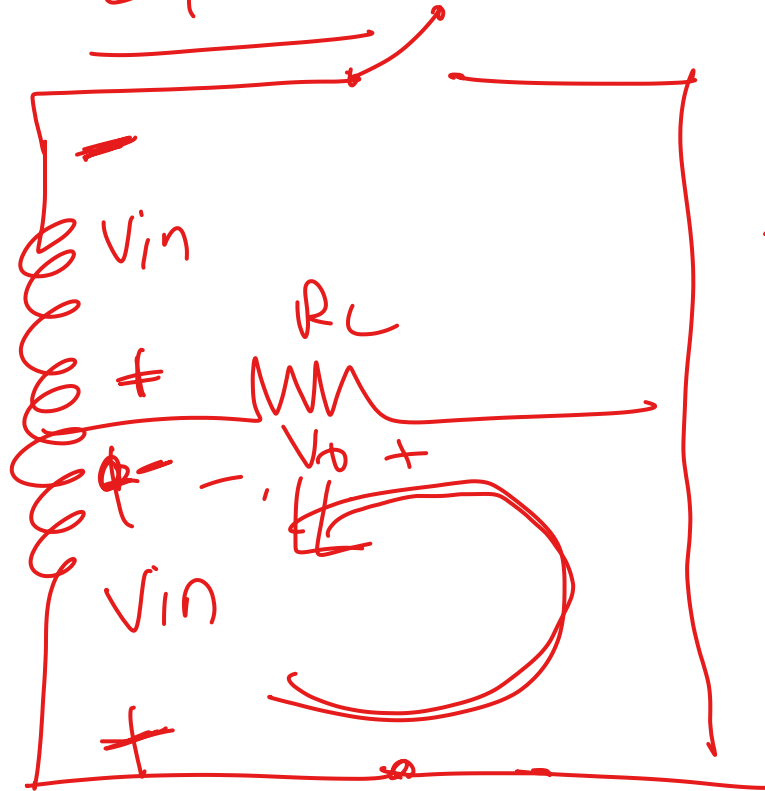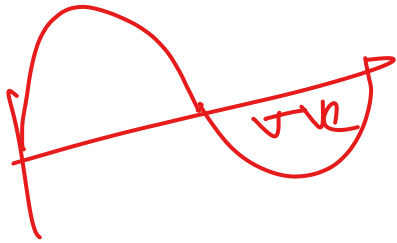$\underline{D_1 \rightarrow RB} \rightarrow \text{open}$



Average Vtg :-

$$\text{HWR } V_{avg} = \frac{V_m}{\pi}$$

$$\frac{\text{FWR}}{V_{avg}} = \frac{2V_m}{\pi}$$

$$\text{HWR } V_{avg} = 5V$$

$$\text{FWR } V_{avg} = 2 \times 5 = 10V$$


$$V_{avg} = \frac{2(V_m - 0.7)}{\pi} \text{ (si)}$$

$$V_{avg} = \frac{2(V_m - V_T)}{\pi}$$

2) Peak Inverse Vtg



$$PIV = 2V_m$$

2) Full wave Bridge Rectifier ckt:-

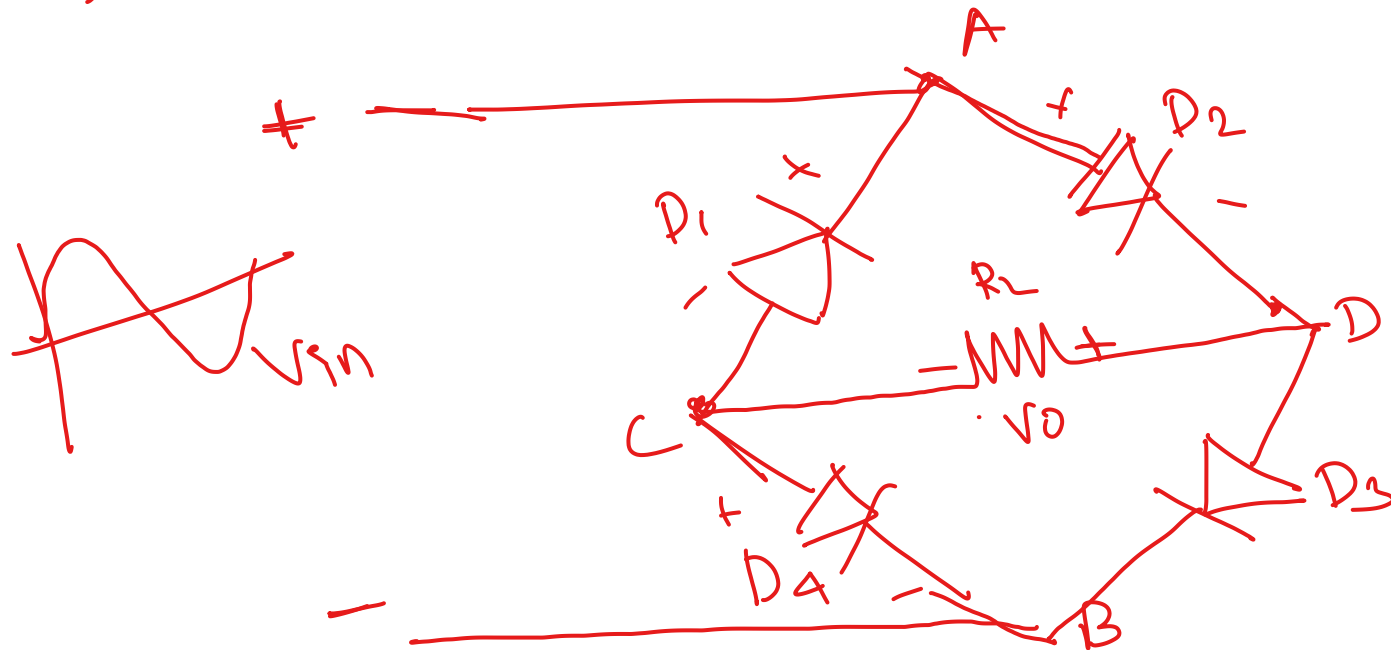

1st half cycle

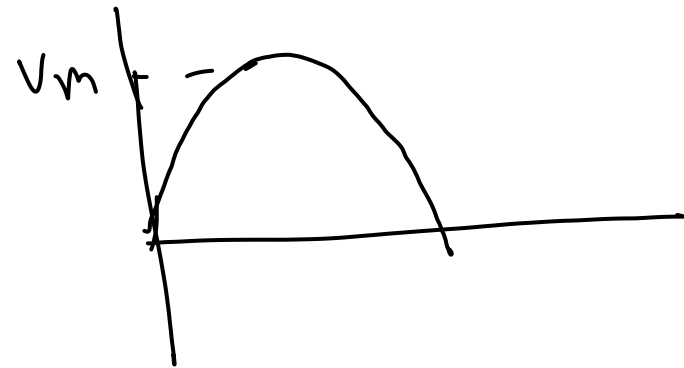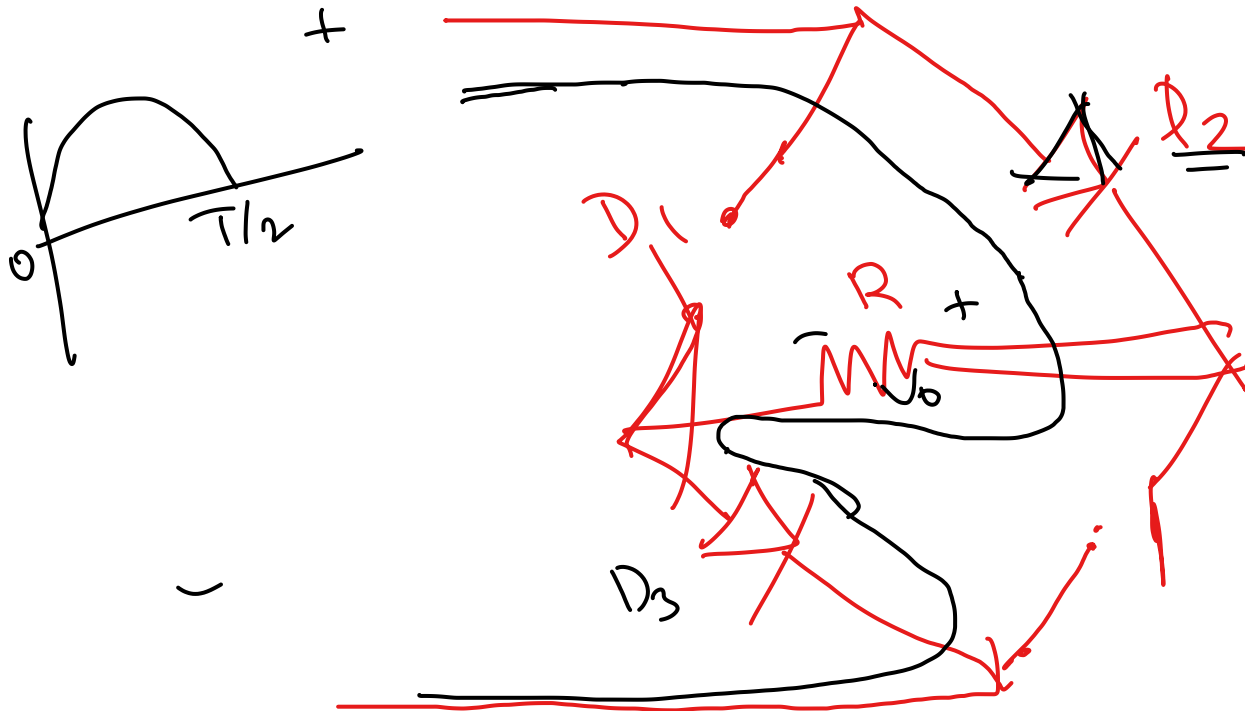$D_2 \quad D_4 \Rightarrow FB \quad ON$
 $D_1 \quad D_3 \Rightarrow RB \quad OFF$





2nd half cycle

RB


D₂ & D₄ OFF

D₁ & D₃ FB ON

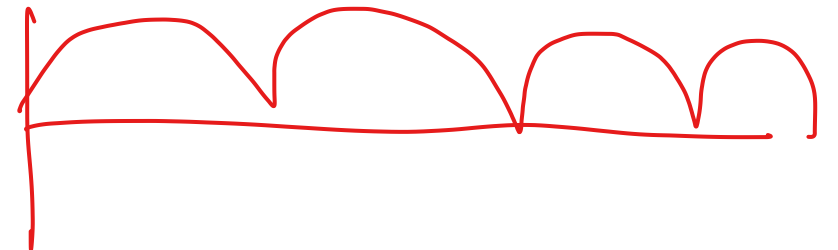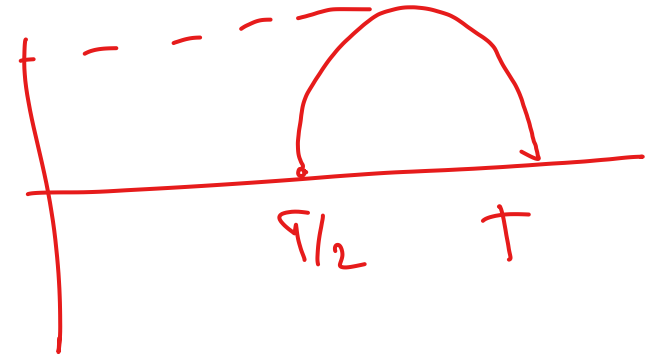

$$V_{avg} = \frac{2V_m}{\pi} \quad (\text{ideal})$$
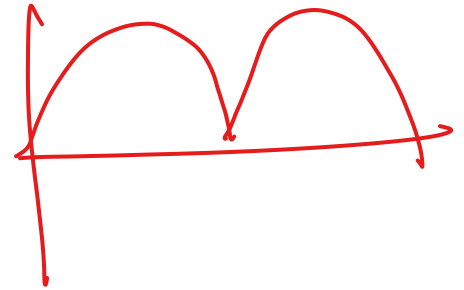
$$V_{avg} = \frac{2(V_m - \underline{2V_T})}{\pi}$$



$$\eta = 0.71$$

$$U_r = 0.3V$$

3) Peak Inverse Voltage

$$PIV = V_m$$

4) Ripple factor .

$$r = \frac{V_{rms}}{V_{dc}} = \frac{0.43}{\text{(without filter)}}$$

1.21

Half wave

With filter

$$r = \frac{V_{rms}}{V_{dc}} = \frac{1}{4\sqrt{3} f R_L C}$$

Efficiency

$$\eta = \frac{\text{DC Output power}}{\text{AC Input power}}$$
$$= \underline{\underline{81.2\%}}$$

HWR
40.6%

Summary

Performance	Center tapped Transformer	Bridge Rectified	AWR
<u>PIV</u>	$2V_m$	V_m	V_m
Output frequency	$2f$	$2f$	f
Ripple factor	0.43	0.43	1.21
Efficiency	81.2%	81.2%	40.6%

RMS Value

$$V_m / \sqrt{2}$$

Average Value
(dc Value)

$$\frac{2(V_m - V_T)}{\pi}$$

$$V_m / \sqrt{2}$$

$$V_m / \sqrt{2}$$

$$\frac{2(V_m - \underline{2V_T})}{\pi} \quad \left| \frac{V_m}{\pi} \right.$$



.



.



.



.



.



.



.



.